

Parts Export

Generated: 2026-06-10 07:20:24

Total Parts: 5

Image	Part Number	Name	Category	Manufacturer	Description	Specification	Tags
No Image	EDD-00005-A	5Volt regulator	ED - Electronic Device	Texas Instruments, STMicroelectronics, ON Semiconductor, Fairchild Semiconductor	LM7805 TO-92 voltage regulator device designed to provide stable 5V DC output for electronic circuits, embedded systems, sensors, and microcontroller applications. It regulates higher input voltage into a constant 5V output with built-in thermal overload and short-circuit protection for reliable operation. Commonly used in Arduino projects, power supply circuits, IoT devices, educational electronics kits, and low-power embedded systems.	Device Type: Linear Voltage Regulator Output Voltage: 5V DC Package Type: TO-92 Input Voltage Range: 7V – 20V Output Current: Up to 100mA	LM7805 • voltage regulator • 5V regulator • TO-92 regulator • linear regulator • power supply IC
No Image	EDD-00005-B	12Volt regulator	ED - Electronic Device	Texas Instruments, STMicroelectronics, ON Semiconductor, Fairchild Semiconductor	LM7812 TO-92 voltage regulator device designed to provide stable 12V DC output for electronic circuits, embedded systems, communication modules, and power supply applications. It regulates higher input voltage into a constant 12V output with built-in thermal overload and short-circuit protection for reliable operation. Commonly used in power management circuits, robotics systems, Arduino projects, industrial electronics, and educational embedded applications.	Device Type: Linear Voltage Regulator Output Voltage: 12V DC Package Type: TO-92 Input Voltage Range: 14V – 30V Output Current: Up to 100mA	voltage regulator • TO-92 regulator • linear regulator • power supply IC • LM7812 • 12V regulator
No Image	EDD-00005-C	6Volt regulator	ED - Electronic Device	Texas Instruments, STMicroelectronics, ON Semiconductor, Fairchild Semiconductor	LM7806 TO-92 voltage regulator device designed to provide stable 6V DC output for electronic circuits, embedded systems, sensors, and low-power applications. It regulates higher input voltage into a constant 6V output with built-in thermal overload and short-circuit protection for reliable and safe operation. Commonly used in Arduino projects, battery-powered systems, robotics circuits, educational electronics kits, and embedded development applications.	Device Type: Linear Voltage Regulator Output Voltage: 6V DC Package Type: TO-92 Input Voltage Range: 8V – 20V Output Current: Up to 100mA	voltage regulator • TO-92 regulator • linear regulator • power supply IC • LM7806 • 6V regulator
No Image	EDK-00003-A	transistors	ED - Electronic Device	ON Semiconductor, Fairchild Semiconductor, Toshiba, NXP Semiconductors	TO-92 transistor kit containing multiple commonly used NPN and PNP transistors for switching, amplification, signal processing, and embedded electronics applications. It provides a compact assortment of semiconductor devices suitable for prototyping, Arduino projects, educational electronics, robotics systems, and circuit development work. Commonly used in amplifier circuits, sensor interfacing, motor control, switching applications, and DIY electronics projects.	Package Type: TO-92 Transistor Types: NPN and PNP Operating Voltage: Up to 60V Current Rating: Up to 800mA Current Rating: Up to 800mA	transistor kit • TO-92 transistor • NPN transistor • PNP transistor • semiconductor kit • switching transistor
No Image	EDK-00006-A	Diode and Transistor Kit	ED - Electronic Device	ON Semiconductor, Vishay, STMicroelectronics, Fairchild Semiconductor	Diode and transistor kit containing a selection of commonly used semiconductor components including rectifier diodes, signal diodes, Zener diodes, NPN and PNP transistors for electronics prototyping and circuit development. It provides essential components for switching, signal control, rectification, voltage regulation, and amplification in embedded systems.	Kit Type: Semiconductor Assortment Kit Components Included: Diodes (Rectifier, Signal, Zener), NPN & PNP Transistors Max Voltage: Up to 1000V (depending on component) Max Current: Up to 3A (depending on component)	transistor kit • NPN transistor • semiconductor kit • diode kit • rectifier diode • Zener diode